

Lighting Basics for Modeling Applications by Jim Osborn, MMR®



Lighting Basics for Modeling Applications


Today's Topics

- Bulbs vs. Light Emitting Diodes (LEDs)
- Properties of Components
- How to Wire various LED Circuits
- Selecting LEDs
- Interior Lighting Installation Example
- Tools & Components Glossary
- Commercially available Hobby Lighting
- Photo Gallery of Examples
- Reference information

Filament Bulb Properties

Filament Bulbs – AKA Grain of wheat bulbs

- Desirable shape for certain applications – Pole lights, shed lights, under a light shade, etc.
- Bulbs have a nice warm incandescent color temperature.
- Bulbs are voltage controlled. More voltage yields a brighter light output – but lowers its life.
- Bulbs will require replacement.
- Cold filament inrush current kills the bulbs. A slow voltage ramp-up circuit will extend their life.
(See ref. notes)

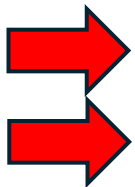

Filament Bulb Properties


Filament Bulb Application







Filament Bulb Properties

Wiring Basics

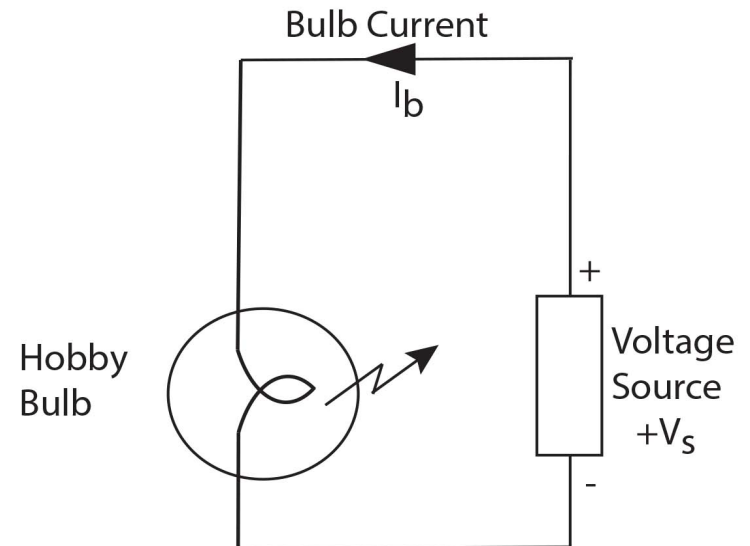
- A filament bulb is a voltage-controlled device.
- Do not exceed the bulb voltage rating
- Higher voltage > Brighter light > shorter life.
- Bulbs can be run off ac or dc power.
- Bulbs come in a variety of size, voltage and current ratings.



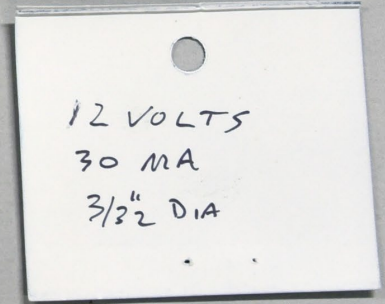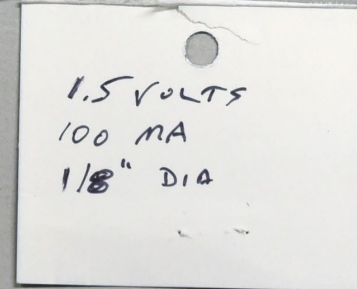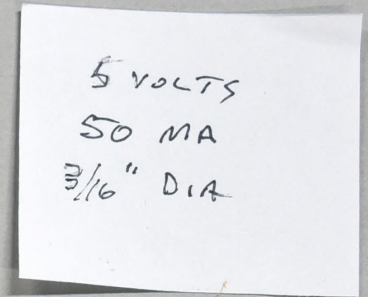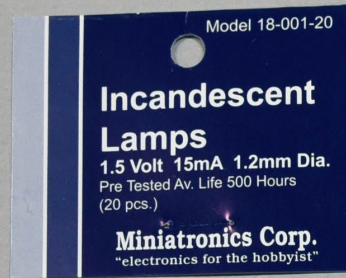

LED Properties

The Versatile LED

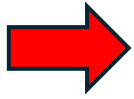

- Very long life-time.
- Cooler and often use less power than bulbs.
- Available in a variety of colors.
- Can be tinted with glaze paints.
- Great for many applications like streetlights, over door fixtures, ceiling lights, and other space restricted locations.
- Some have multiple colors built in.
- Many shapes & sizes.

+
RED
5mm
RED/GRN

+
RED
3mm
RED/GRN

+
RED
3mm
RED/GRN
w/ common

+ -
3mm
YELLOW
GLOW

+ -
3mm
YELLOW GLOW

+ -
5mm
RED

-
1.2mm

+ -
5mm
GREEN


+ -
3mm
RED

+ -
3mm
YEL




+ -
3mm
GRN

+ -
2mm
TOWER
YEL-GLO





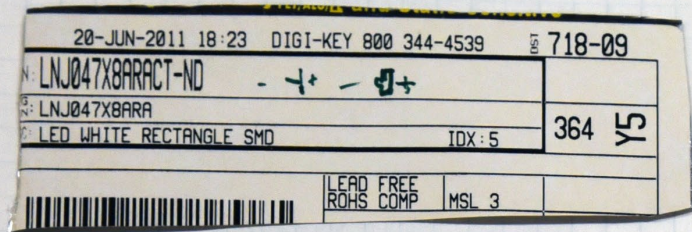


1.5 mm white
10 ma.

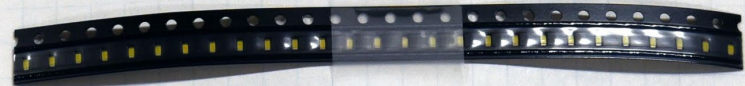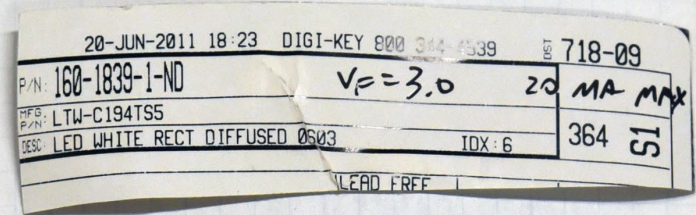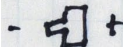

2.0 mm white
20 ma.

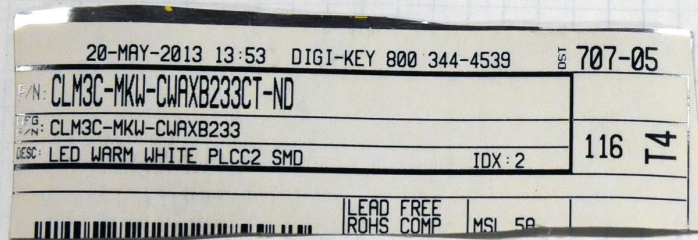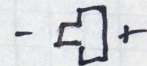

3.0 mm soft white
20 ma.

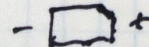

Surface Mounted LEDs (SMD)







Pre-wired SMDs


2.0 mm

RED = +
GRN = -


1.5 mm

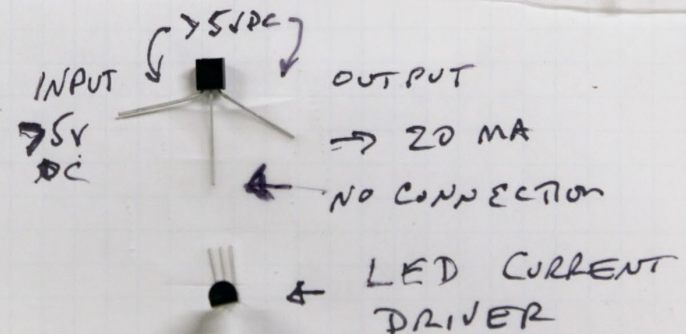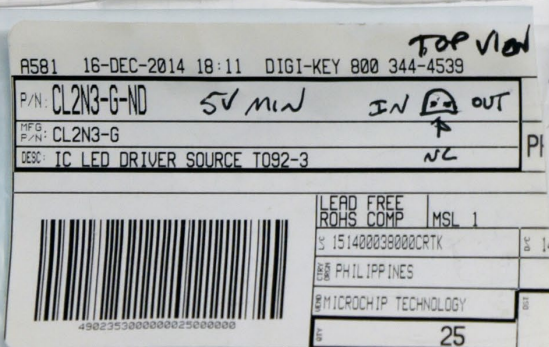


Electronics Basics – Ohm's Law

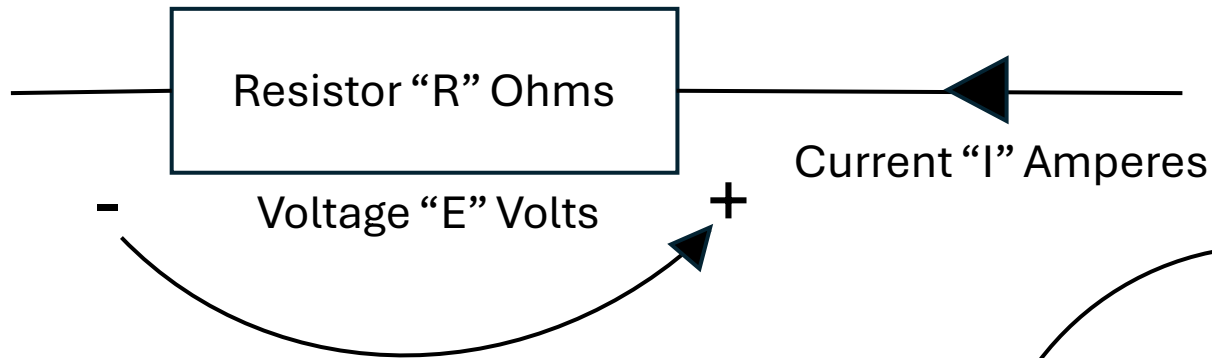

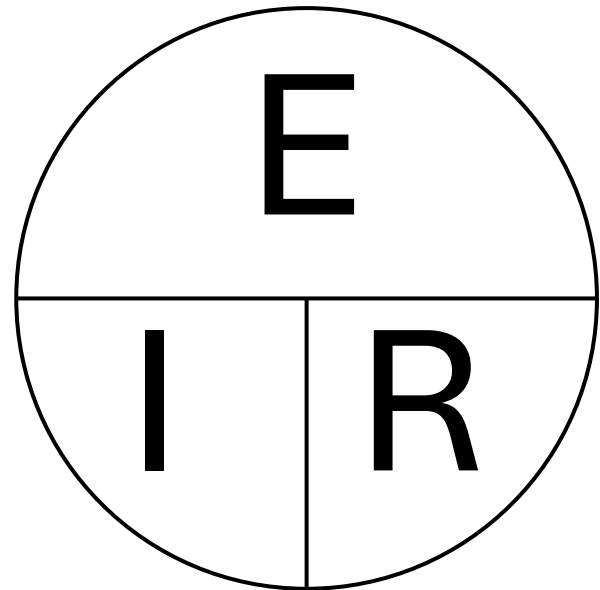
- Ohm's Law $E = I \times R$
- Remember this simple Icon
- Cover the element you're solving for
- The remaining symbols define the ratio




Electronics Basics – Ohm's Law

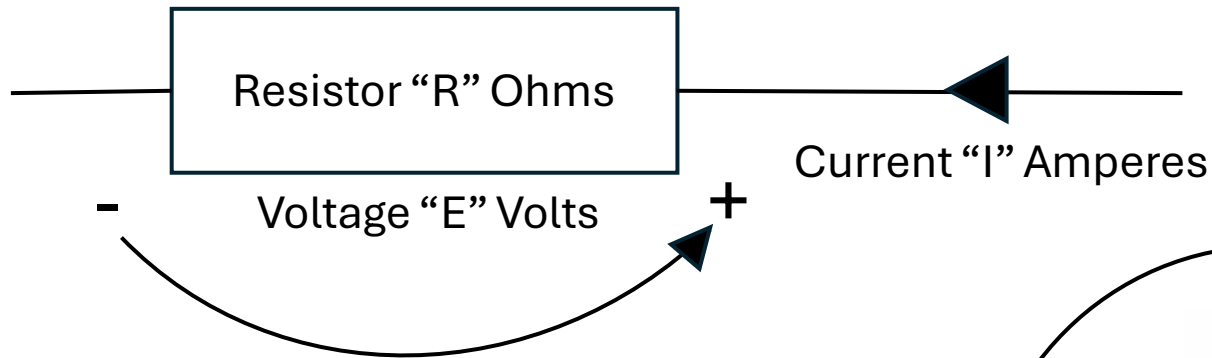

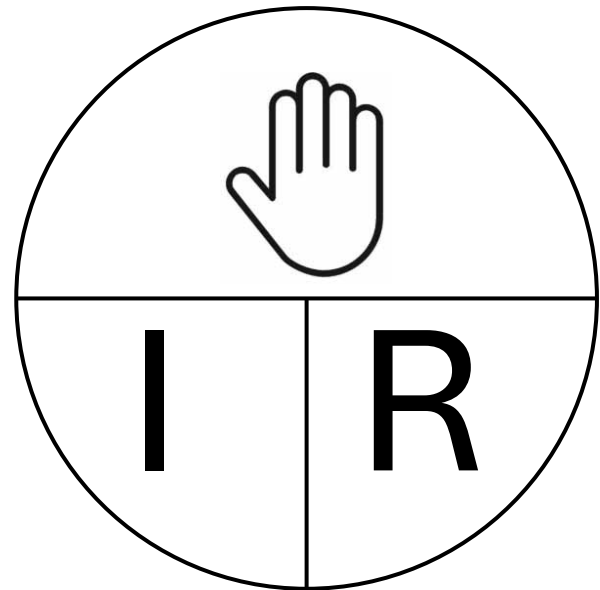
- Ohm's Law $E = I \times R$
- Remember this simple Icon
- Cover the element you're solving for
- The remaining symbols define the ratio




Electronics Basics – Ohm's Law

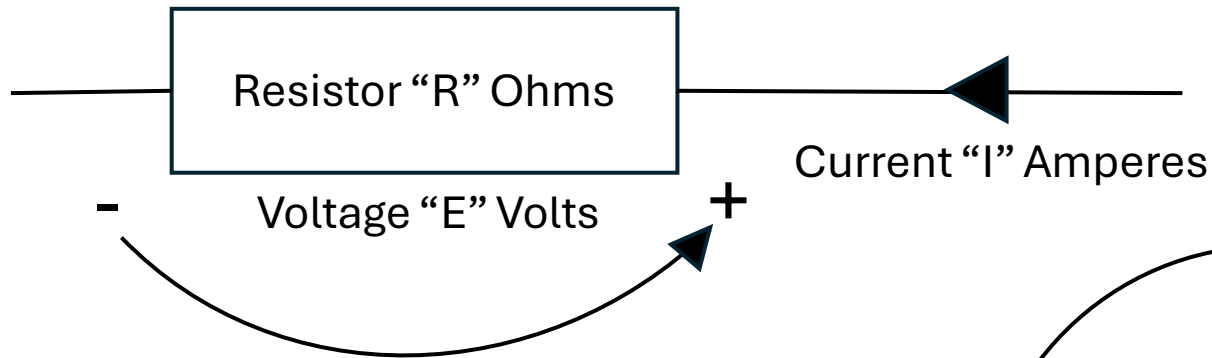

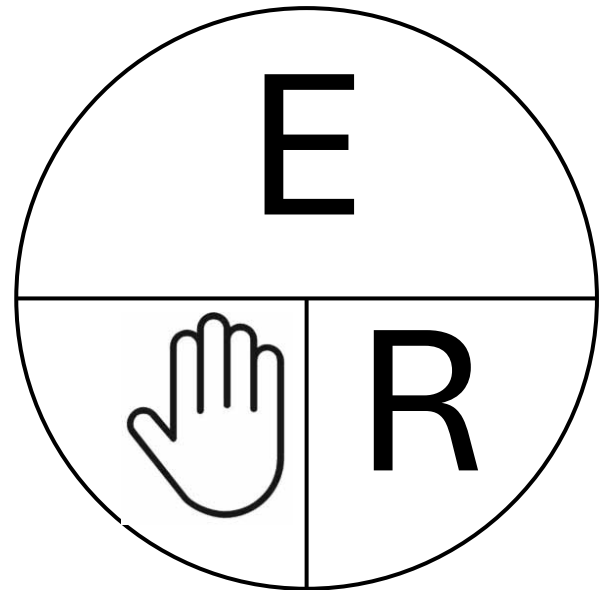
- Ohm's Law $E = I \times R$
- Remember this simple Icon
- Cover the element you're solving for
- The remaining symbols define the ratio



Electronics Basics – Ohm's Law

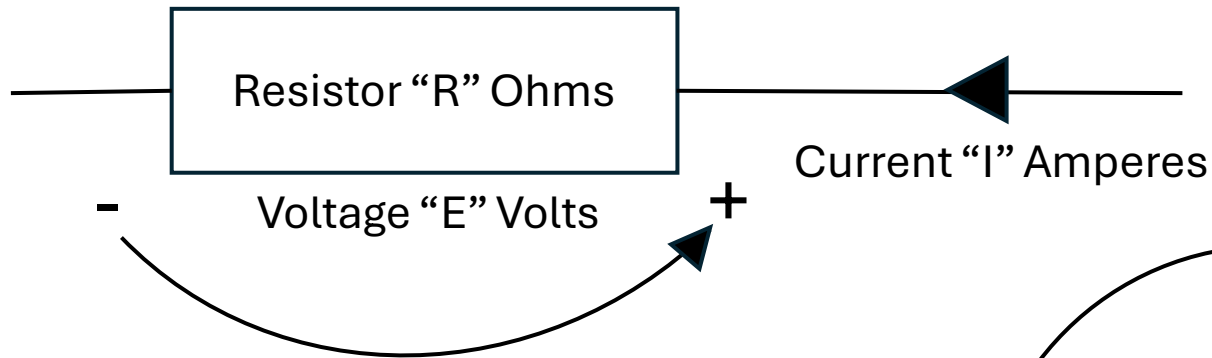

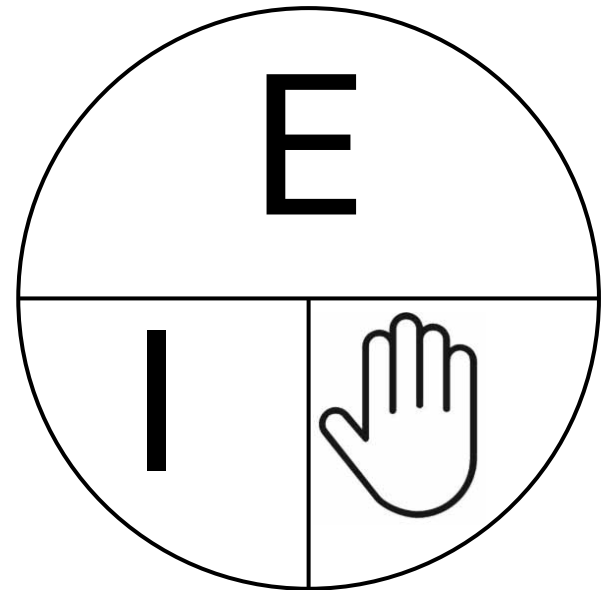- Ohm's Law $E = I \times R$
- Remember this simple Icon
- Cover the element you're solving for
- The remaining symbols define the ratio



LED Properties


LED Applications



LED Properties

LED Wiring Basics

- Current controlled device not voltage controlled like a bulb.
- Brightness is a function of the current flowing through it.
- More current yields a brighter light output.
- Most will usefully illuminate with 5 to 20 milliamps (ma) current flow.
- White LEDs have a max continuous current rating of 20 ma and a voltage drop of approximately 3 volts.
- DO NOT apply a voltage source directly across the LED. You will likely kill it!
- The wattage rating of the series resistor needs to be calculated.

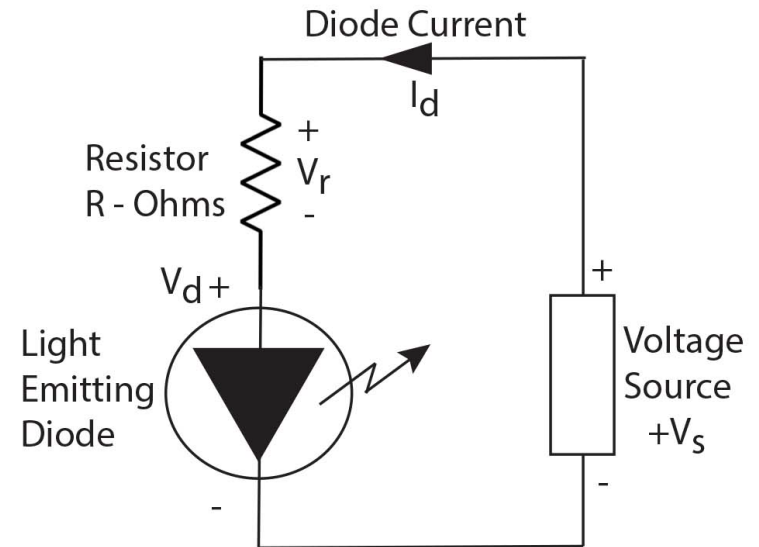

Governing Equations

$$V_s = V_r + V_d$$

or

$$V_r = V_s - V_d$$

Need to calculate R

$$V_r = I_r \times R \text{ (Ohm's law)}$$

or

$$R = V_r / I_d$$

Power dissipated in R

$$P_r = I_d \times I_d \times R \text{ (watts)}$$

LED Properties


LED Wiring Basics Example 1

➡ The value of resistor R sets the current through the LED.

If $V_s = 12 \text{ volts}$ and $V_d = 3 \text{ Volts}$, then V_r will = 9 volts

If we want I_d to = **.02 amps (20 ma)** then **$R = 450 \text{ ohms}$**
(470 ohms is a standard value)

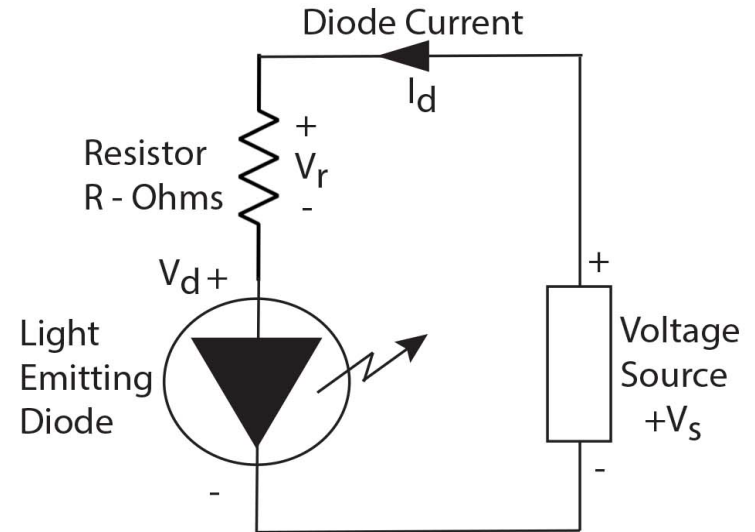Resistor wattage = 0.18 watts (Use a ½-watt resistor. Design practice is to keep resistor dissipation to half its rated value.)



Governing Equations

$$V_s = V_r + V_d$$

or

$$V_r = V_s - V_d$$

Need to calculate R
 $V_r = I_r \times R$ (Ohm's law)

or

$$R = V_r / I_d$$



Power dissipated in R
 $P_r = I_d \times I_d \times R$ (watts)


LED Properties

LED Wiring Basics Example 2

If $V_s = 12 \text{ volts}$ and $V_d = 3 \text{ Volts}$, then V_r will = 9 volts

If we want I_d to = **.01 amps (10 ma)**
then **$R = 900 \text{ ohms}$**
(1000 ohms is a standard value)

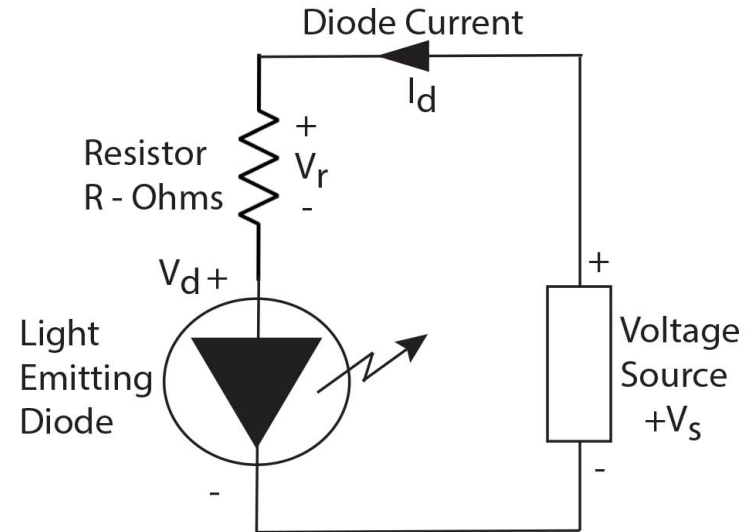Resistor wattage = 0.09 watts
(1/4-watt resistor will do)



Governing Equations

$$V_s = V_r + V_d$$

or

$$V_r = V_s - V_d$$

Need to calculate R
 $V_r = I_r \times R$ (Ohm's law)

or

$$R = V_r / I_d$$



Power dissipated in R
 $P_r = I_d \times I_d \times R$ (watts)


LED Properties

LED Wiring Basics Example 3

If $V_s = 5 \text{ volts}$ and $V_d = 3 \text{ Volts}$, then V_r will = 2 volts

If we want I_d to = **.02 amps (20 ma)** then **$R = 100 \text{ ohms}$** .

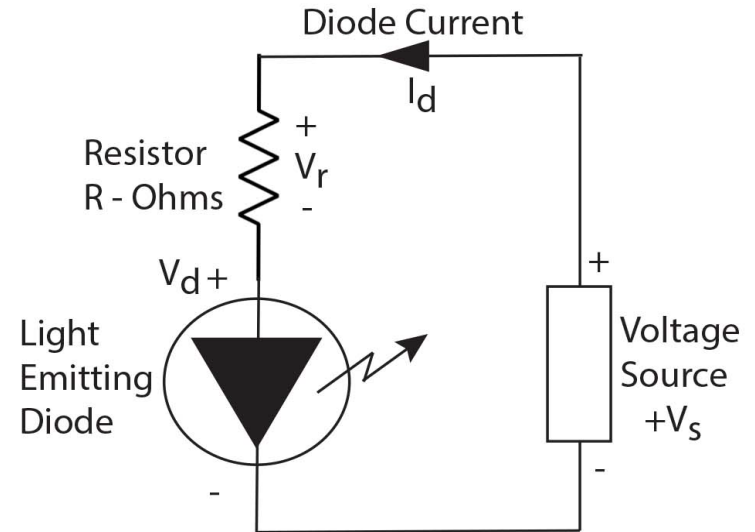Resistor wattage = 0.04 watts
(1/8 or 1/4-watt resistor)



Governing Equations

$$V_s = V_r + V_d$$

or

$$V_r = V_s - V_d$$

Need to calculate R

$$V_r = I_r \times R \text{ (Ohm's law)}$$

or

$$R = V_r / I_d$$


Power dissipated in R

$$P_r = I_d \times I_d \times R \text{ (watts)}$$

LED Properties

LED Wiring **LED Driver** - Example 4

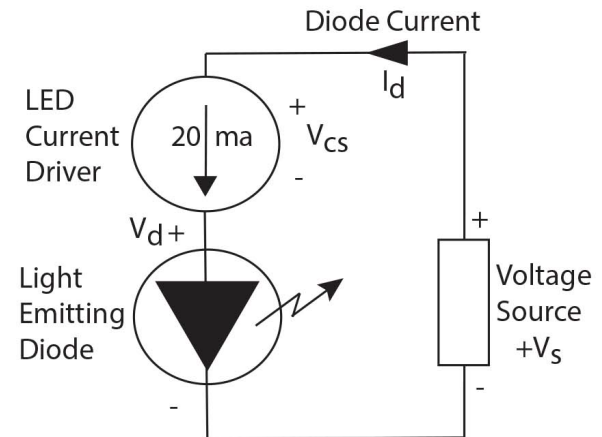- An **LED Driver** replaces the resistor in the LED circuit
- An **LED Driver** supplies a constant current if its minimum voltage is maintained.
- Small LED drivers require at least 5 volts across them.
- In this example the driver supplies 20 ma to what ever is connected to it.
- A quick and easy LED circuit.



Current Source Governing Equations

$$V_s = V_{cs} + V_d$$

Voltage across the current source
must be > 5.0 volts, so --
 V_s must be $> 5.0 + V_d$




Assume $V_d = 3.0$ volts
therefore V_s must be
greater than 8 volts

LED Properties

LED Wiring **LED Driver** - Example 5

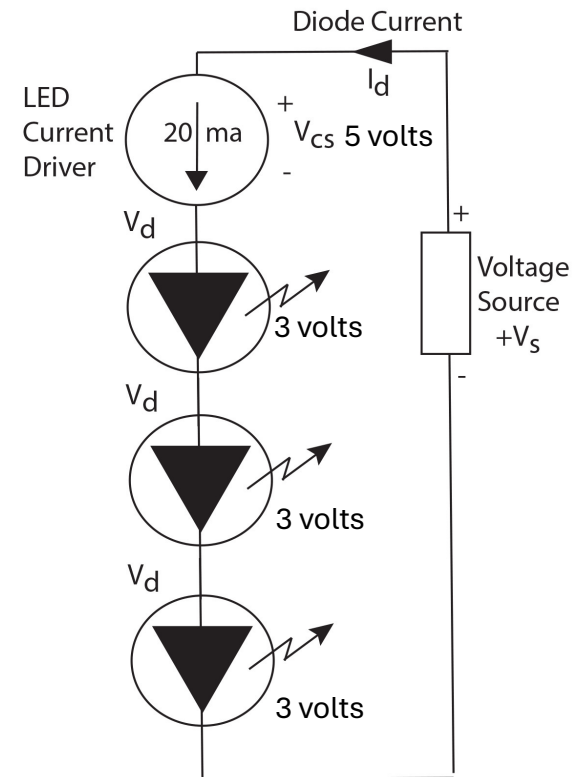
- In this example the driver supplies 20 ma to what ever is connected to it.
- A quick and easy LED circuit.
- There is no limitation on the number of LEDs added as long as the minimum driver voltage is maintained at greater than 5 volts.
- In this case $V_s = 3 \times V_d + 5$ or
 $3 \times 3 + 5 = 14\text{v}$ or greater



LED Properties

LED Wiring **LED Driver** - Example 6

- An **LED Driver** replaces the resistor in the LED circuit
- In this example the driver supplies 20 ma to what ever is connected to it.
- In this example the 20 ma source current is split down the two LED legs.
- The LEDs should be same to balance the current paths.
- **There is no limitation on the number of LEDs added as long as the minimum driver voltage is maintained. (5 volts)**
- In this case $V_s = 3 \times V_d + 5$ or greater than $3 \times 3 + 5 = 14v$.

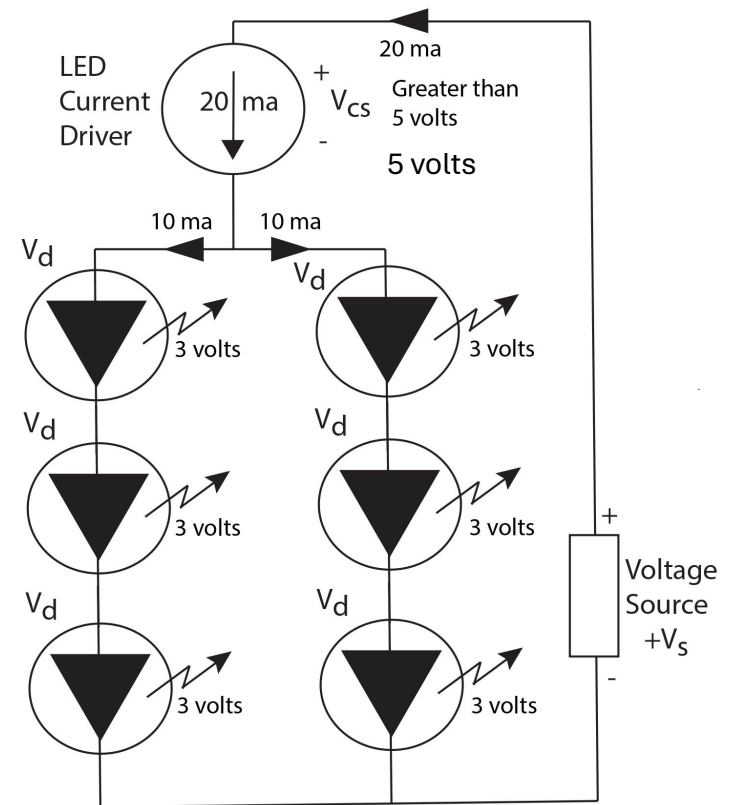


Selecting LEDs

Many choices – Here's a couple suggestions

- For the 1.5 and 2 mm LED sizes I buy pre-wired LEDs
 - they come with or without 9-12v sized resistors
- In most cases use “cool white” LEDs for general lighting
- Over door goose neck lights – 2.0 mm SMD @ 10 ma current flow
- Modern street lights – 2.0 mm SMD @ 20 ma current flow
- Modern In building ceiling lights – 3 mm SMD @ 10 to 20 ma
- Old building lighting – 3 mm SMD @ 10 to 20 ma & orange glaze
- Target signals – 1.5 to 3 mm leaded two color two or three leaded.
 - two leaded bi-color leds require a special driver circuit for yellow.
- 3 light vertical signals – R, Y & G in an appropriate size for the target.
- Panel lights - 5 mm single or bi-color depending on need.
- Turnout indicators – 3 or 5 mm bi-color.

Interior Lighting Installation Example

Let's light up this small shop.

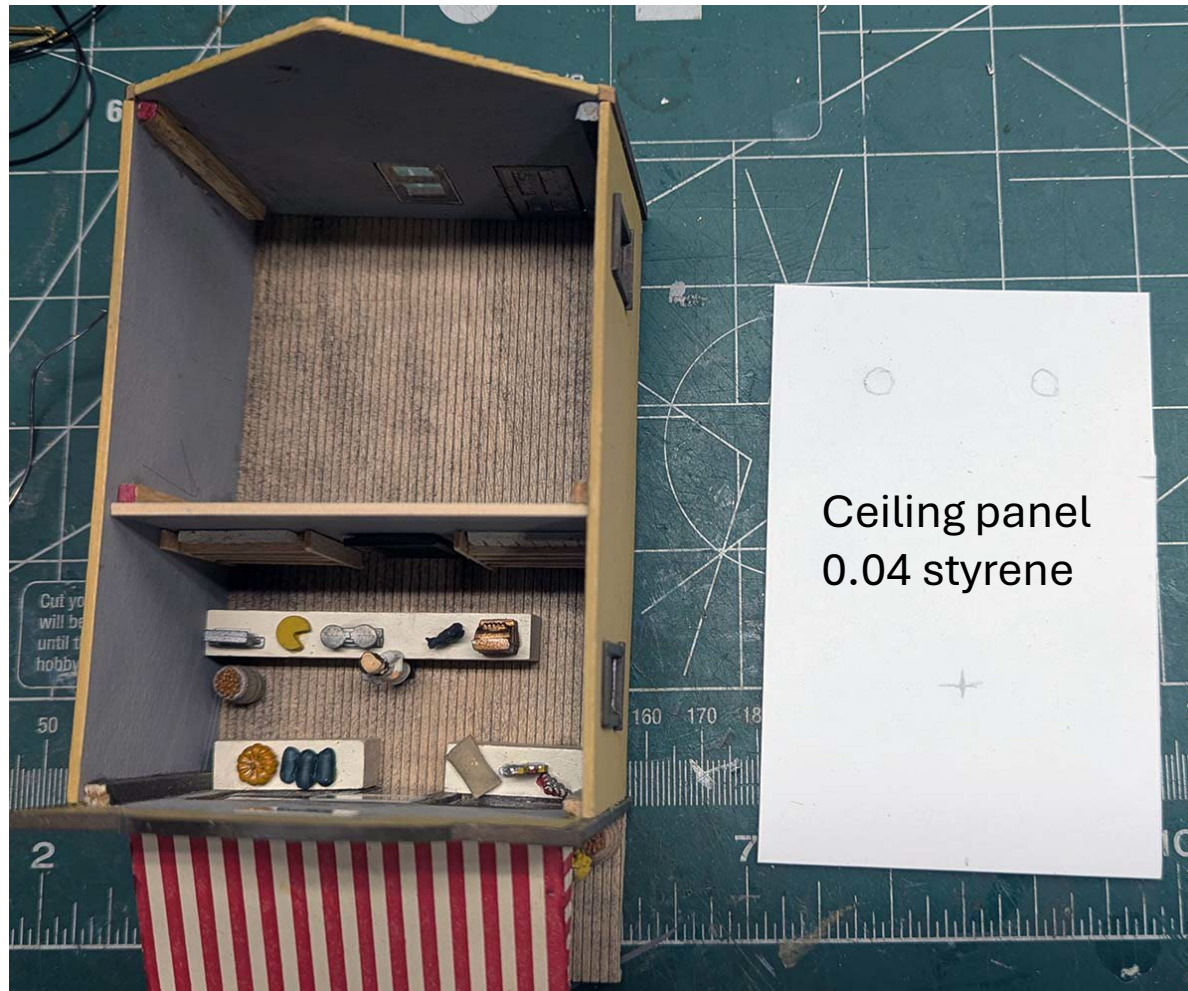


Interior Lighting Installation Example

Copper foil adhesive tape will be used to connect the LEDs




Interior Lighting Installation Example

3 mm SMD LEDs for the ceiling lights

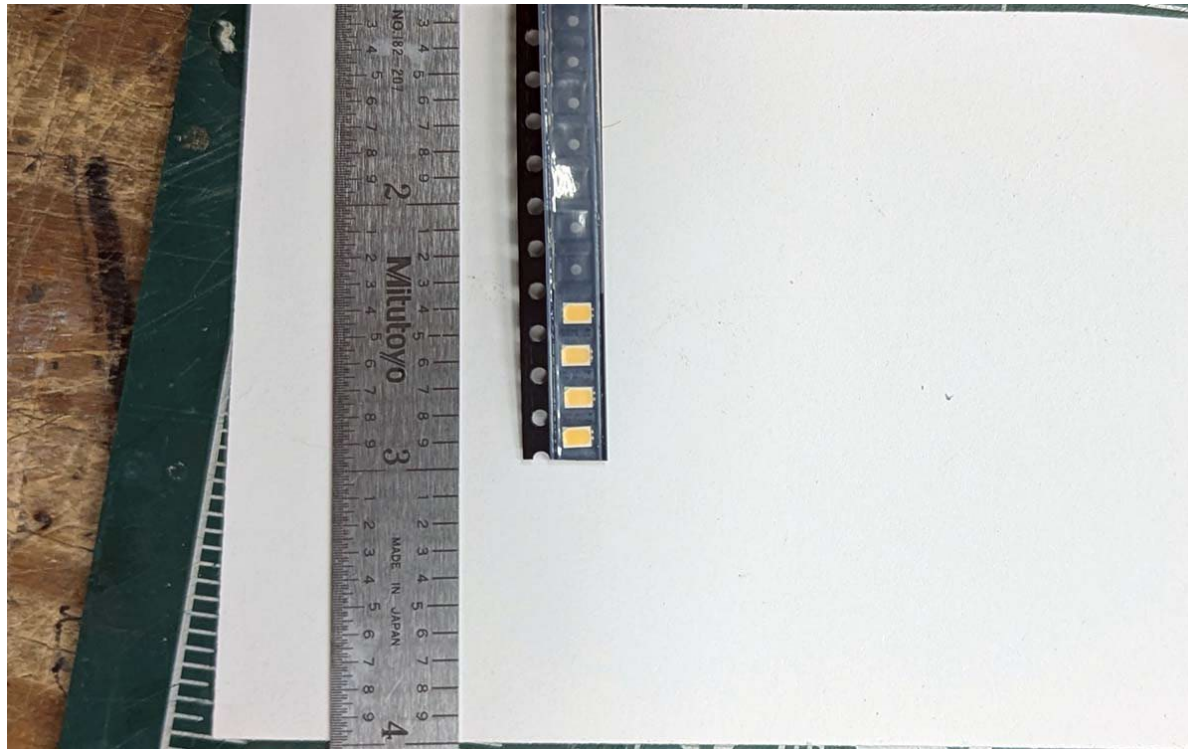


Interior Lighting Installation Example

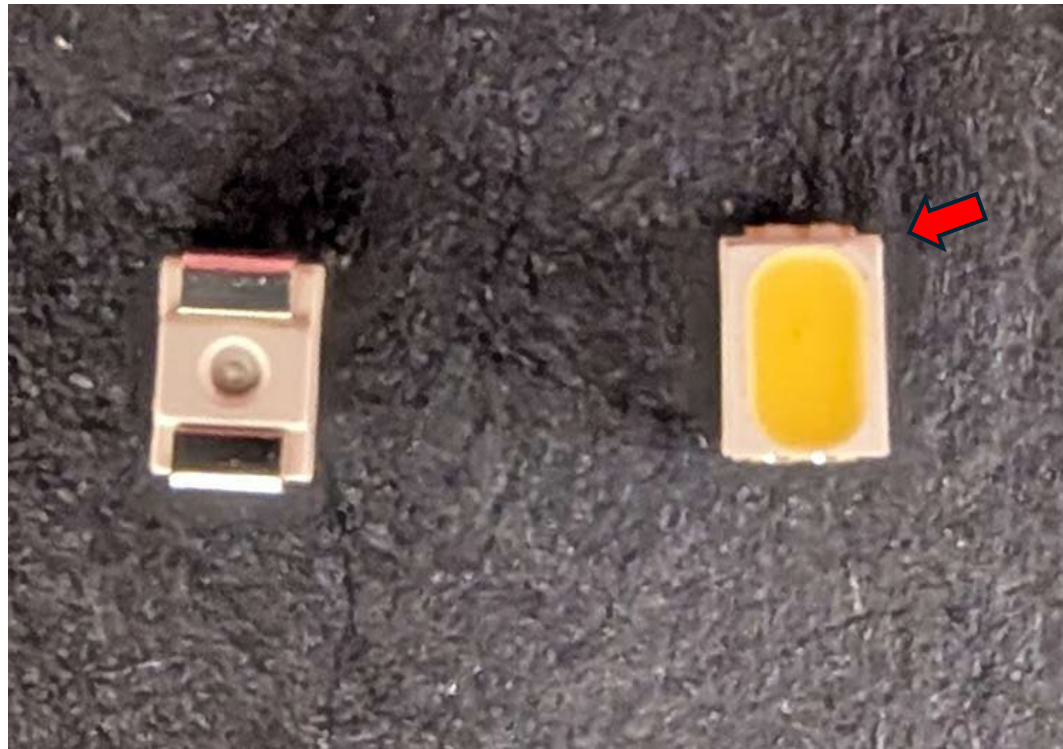Front and back of an SMD LED. Note the notch on the upper right corner that denotes the Anode or + connection.




Interior Lighting Installation Example

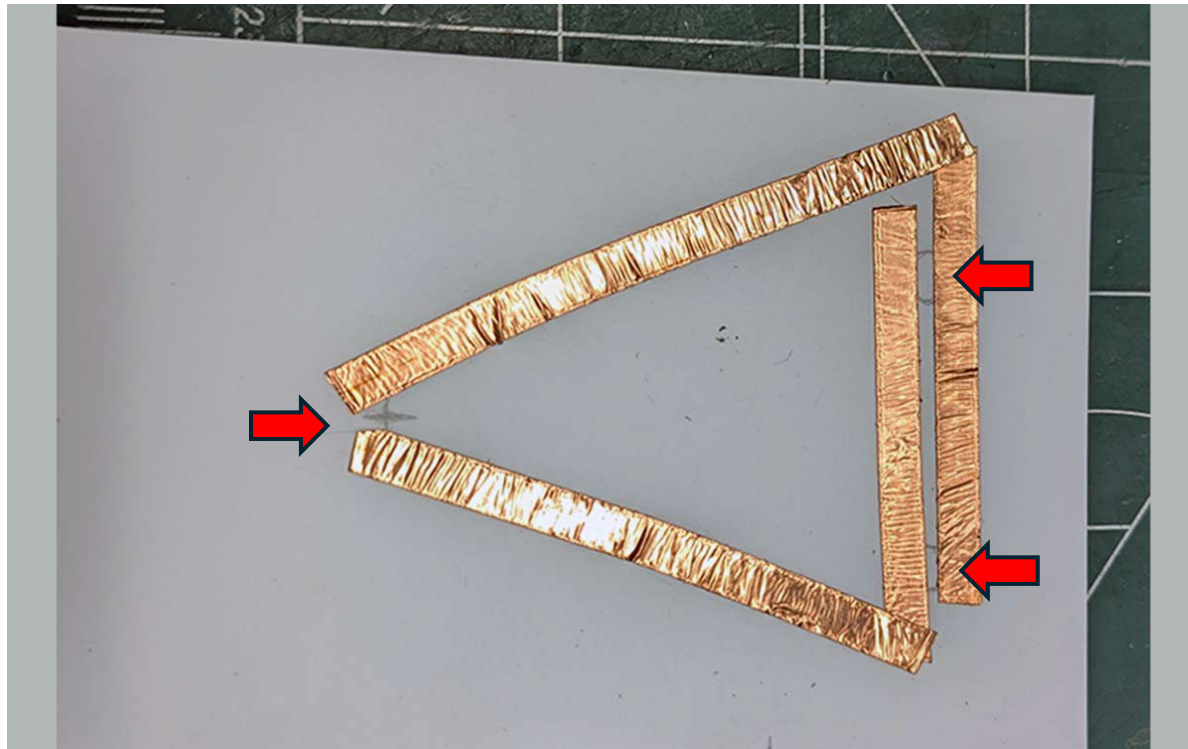The LED positions are marked and the tape applied.
The LEDs will bridge the + and – tape runs.




Interior Lighting Installation Example

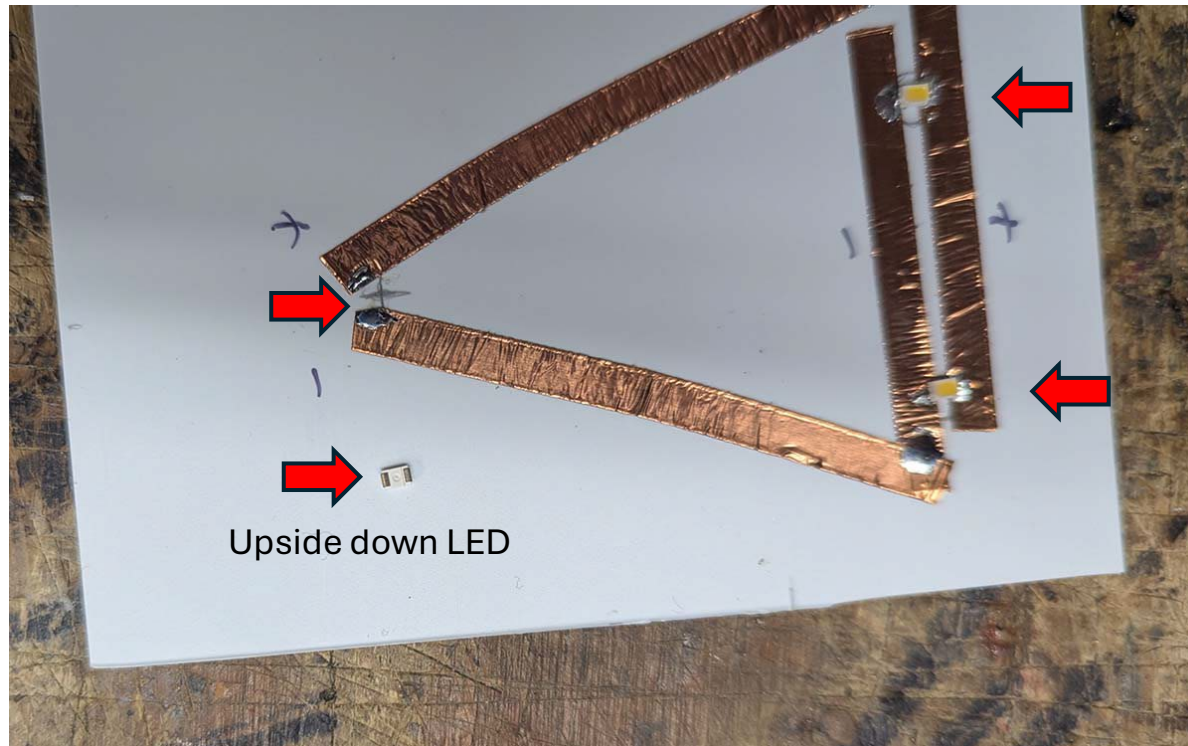The LEDs will bridge the + and – tape runs.
Solder the tape joints and pre tin the LED contact locations. Mark the + and – tape runs.



Interior Lighting Installation Example

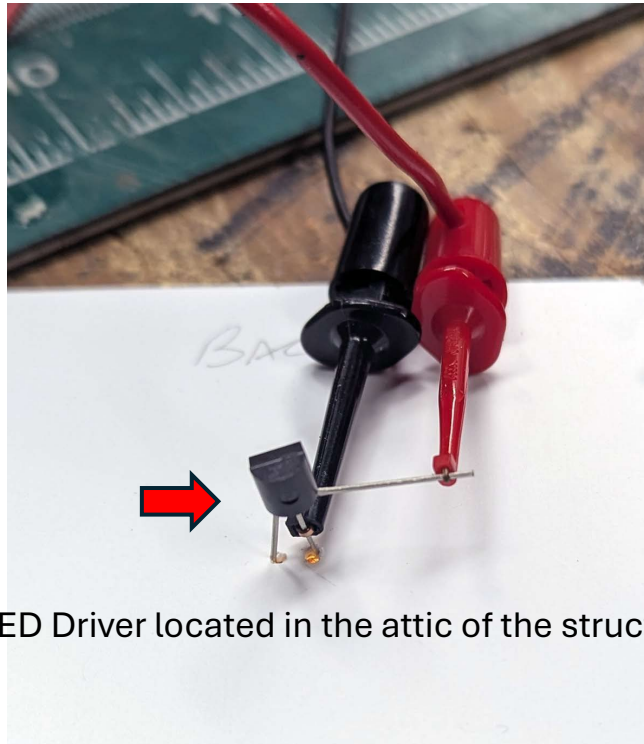Attach a LED driver or resistor on the opposite side of the ceiling panel. Connect the output lead to the + foil tape on the opposite side




LED Driver located in the attic of the structure

Interior Lighting Installation Example

Always test the lights before proceeding.

The LED driver is on the opposite side.

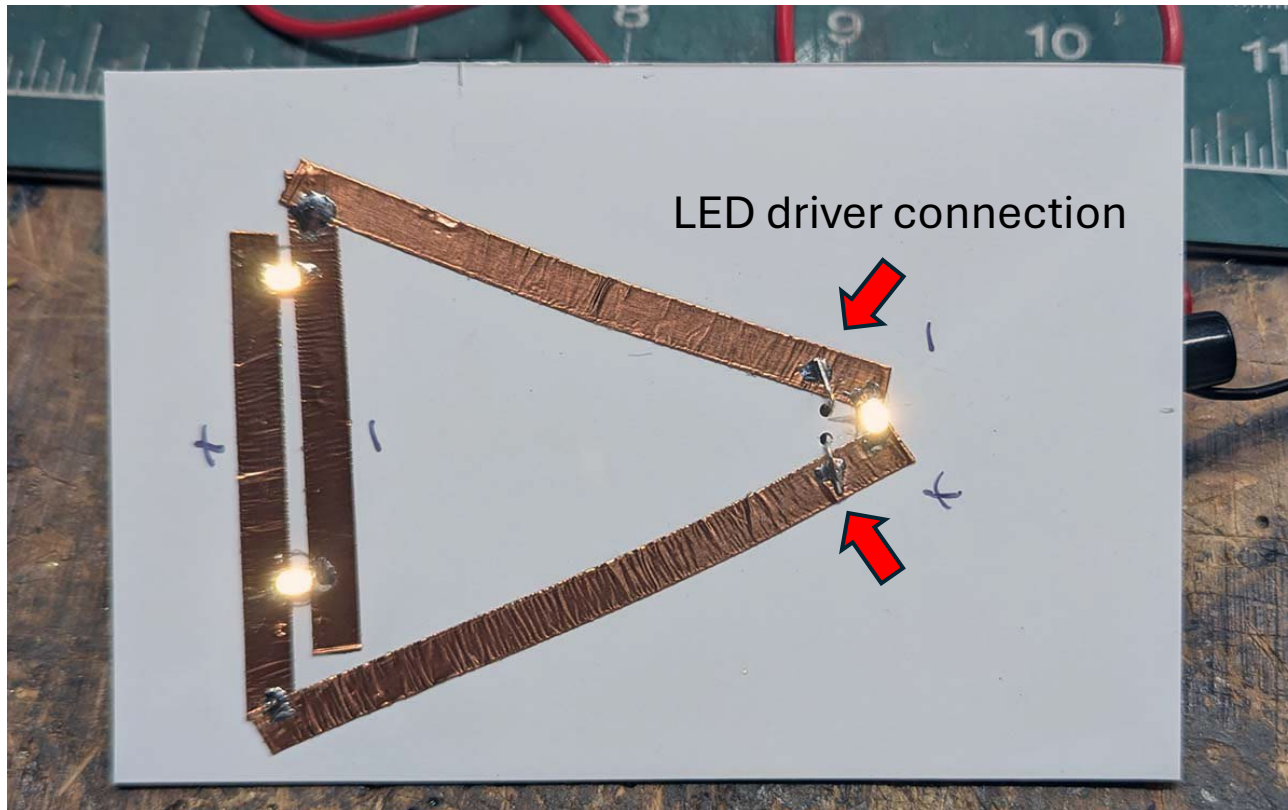


Interior Lighting Installation Example

Prepare the wiring connection for the structure.



Interior Lighting Installation Example

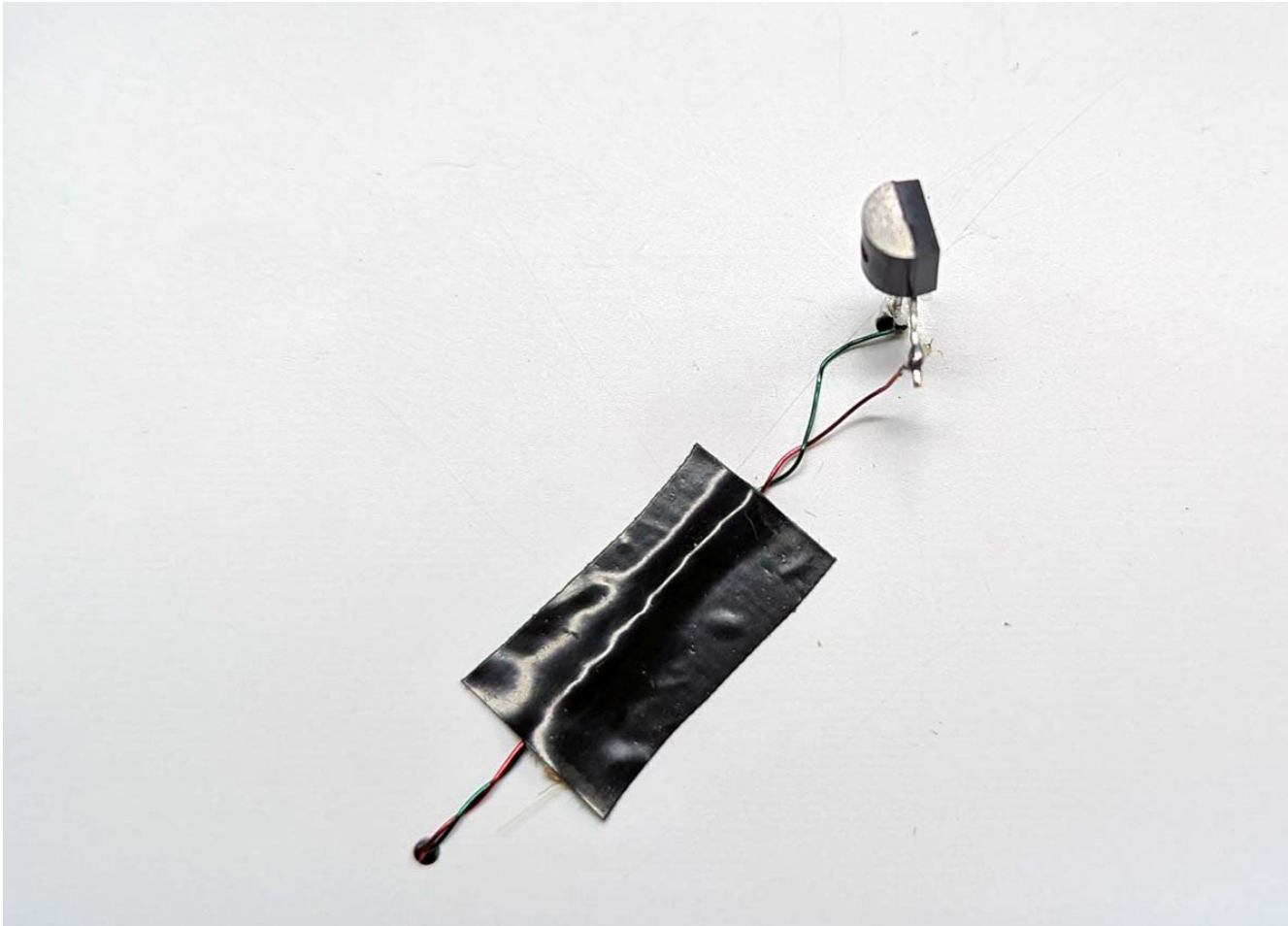Prepare the wiring connection for the structure.



Interior Lighting Installation Example

Fit the lighting panel in the structure and add the roof.



Interior Lighting Installation Example

Open for business!



Tools & Components Glossary

Tools

- 40 watt adjustable heat soldering iron
- Small wet sponge to clean the iron tip
- 0.031 diameter thin rosin core solder
- Fine tipped tweezers & an Xacto knife
- Volt-ohm-ammeter – nothing fancy
- Hemostat clamp - dental pick
- Small drills and pin vises

Soldering

- Keep the iron tip clean – essential!
- Pre-tin the copper tape connections.
- Do not dilly-dally on the copper tape – use a hot iron but be quick.
- Hold down the SMDs with a dental pick, heat the copper for the 1st joint – be quick.
- The second LED connection is easy

Components

- Long life bulbs, lamp shade, other Miniaturics
- Various LEDs , resistors & other DigiKey, Jemco, Mouser
- TO-92 package LED Drivers DigiKey, Jemco, Mouser
- Copper tape – Hobby Lobby ¼ inch
- 30 AWG R/G twisted magnet wire
- Pre-wired LEDs – Evan Designs
- Other LEDs – Evan Designs – D., J., or M.
- Thin tubing, lamp shades, wire & all kinds of lighting stuff
www.ngineering.com
- Tamiya Clear Glazes Red, Orange and Green. Orange makes a nice incandescent lamp.

Woodland Scenics has a very broad selection on pre-configured lighting accessories – and it's Plug n Play!



Commercially available Hobby Lighting – to Name a Few.

Woodland Scenics Just Plug Lighting System

- Traffic Lights
- Vehicles
- Street Lights
- Train Yard Lights
- Wall Mount Lights
- Pre-lit Buildings
- LED Lights
- Bill Boards

Walthers Lighting Categories

- Street Lights
- Signals
- Passenger car interiors
- Buildings
- Wall mount
- Grade Crossing Signals

Commercial Street Lighting in Use



Photo Gallery – Team Track



Photo Gallery – Sterling Station



Photo Gallery – Auction House



Photo Gallery – Patrone Ready-Mix



Photo Gallery – Icing Ramp



Photo Gallery – Gravel City



Photo Gallery – Lumber Yard Workshop



Photo Gallery – Flower Shop



Photo Gallery – Row Houses

Jerry Marci's Pennsylvania Horseshoe Curve RR




Photo Gallery – Fire Station



Photo Gallery – Wheel Works



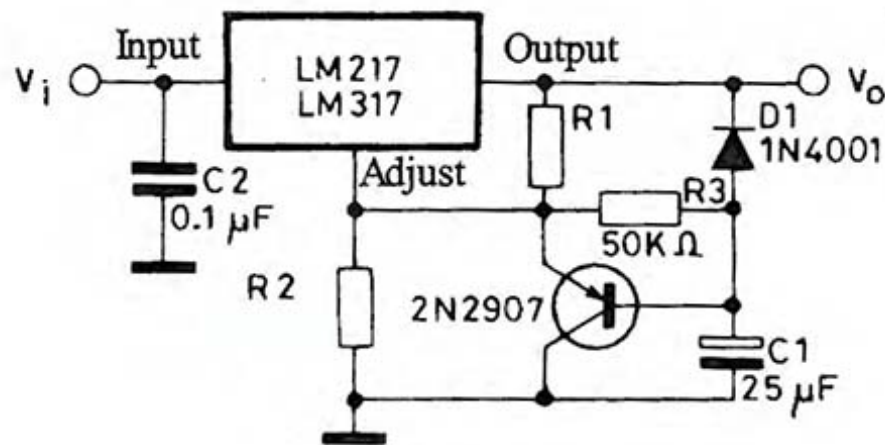Reference Sheet – Slow turn-on Power Supply



Slow Turn-on Regulator

For 1.5v output

$R_1 = 2700 \text{ Ohms}$

$R_2 = 540 \text{ Ohms}$

(Adjustable)

For 12v output: $R_2 = 2200 \text{ Ohms}$ (adjustable) & $R_1 = 270 \text{ Ohms}$

For 10v output: $R_2 = 2000 \text{ Ohms}$ (adjustable) & $R_1 = 270 \text{ Ohms}$

Reference Sheet – LED Resistor Calculator

LED Dropping resistor calculator

Series resistor values given LED forward voltage drop as entered in the brown box below.

LED forward voltage drop = 3.0 volts

DC Supply Voltage	LED Current in milliamps						
	5	7.5	10	12.5	15	17.5	20
5	400	267	200	160	133	114	100
6	600	400	300	240	200	171	150
7	800	533	400	320	267	229	200
8	1000	667	500	400	333	286	250
9	1200	800	600	480	400	343	300
10	1400	933	700	560	467	400	350
11	1600	1067	800	640	533	457	400
12	1800	1200	900	720	600	514	450
13	2000	1333	1000	800	667	571	500
14	2200	1467	1100	880	733	629	550
15	2400	1600	1200	960	800	686	600
16	2600	1733	1300	1040	867	743	650
17	2800	1867	1400	1120	933	800	700
18	3000	2000	1500	1200	1000	857	750
19	3200	2133	1600	1280	1067	914	800
20	3400	2267	1700	1360	1133	971	850

Note: Use the next largest standard resistor value from the calculated chart value.

It is not necessary to be 100% accurate unless you are targeting currents near the 20ma range.

Cell color shows minimum resistor wattage required >> 1/8 watt 1/4 watt 1/2 watt

Ranges of Forward voltage drops for various LED colors

Color	Vf - Min	Vf - Max	Vf - Avg
Infrared	1.6	1.6	1.6
Red	1.6	2.0	1.8
Orange	2.0	2.1	2.1
Yellow	2.1	2.2	2.1
Green	1.9	4.0	3.0
Blue	2.5	3.7	3.1
Violet	2.8	4.0	3.4
Purple	2.5	3.7	3.1
Ultraviolet	3.1	4.4	3.8
Pink	3.3	3.3	3.3
White	2.8	3.5	3.2

Voltages vary by specific LED. These values are from Wikipedia and my own tests. Best to try a value, measure Vf and then recalculate to get the correct value. This is important if you are targeting currents near the 20ma limit value.

Note that most common LEDs have a maximum forward current of 20ma. Some of the micro surface mount LEDs have a continuous rating of 5 ma. Consult a spec sheet for exact operating limits.

Use this link to download your own copy of the calculator

<https://www.foxvalleydivision.org/fvd2016/imagesfvd2016/clinicdata/led-resistor-selection.xlsx>

A Green Board Ahead to light up your Pike!

Any Questions?

